

# EEE 3342C: Digital Systems


## Chapter 7: Multi-Level Gate Circuits NAND and NOR Gates

*Instructor:* Suboh A. Suboh

Department of Electrical Engineering and Computer Science  
University of Central Florida

# Multi-Level Circuits


- This circuit has multiple levels

 

- Let's say the delay of 1 gate is 10 ns (nanosecond)
- The result is available in 40 ns
- When there are more levels, there is more delay


# Sum-Of-Products and Product-Of-Sums

The sum-of-products form has 2 levels.

 

SOP form is also called an  
AND-OR circuit

The product-of-sums form has 2 levels.

 


POS form is also called an  
OR-AND circuit

## Factoring and Multiplying Could Change the Number of Levels

- We have this function
- We draw its diagram without changing the function
- We could reuse (D+E) term


$$Z = AB(D + E) + C(D + E) + ABFG + CFG + H$$

 - If we multiply out, we get:  
 $z = ABD + ABE + CD + CE + ABFG + CFG + H$
- This is a SOP (sum-of-products), it is two level


 
# Cost of a Circuit

- The hardware cost of a circuit is:
  - The number of gates and
  - The total number of inputs



- Number of gates: 6
- Total number of inputs: 13


# Finding the Circuit with the Smallest Cost

- We have the function:  $f(a,b,c,d) = \sum m(1, 5, 6, 10, 13, 14)$
  - We need to find the circuit of  $f$  that has the smallest cost
  - Draw the K-map of  $f$
- 
- 1 Find the minimized SOP expression; find its cost
  - 2 Try to factor it; find its cost
  - 3 Find the minimized POS expression; find its cost
  - 4 Try to factor it; find its cost
- 
- Find the circuit with the smallest cost above the 4 options above

- 1 Find the minimized SOP (sum-of-products) expression; find its cost

| AB   |  |    |    |    |    |
|------|--|----|----|----|----|
| CD \ |  | 00 | 01 | 11 | 10 |
| 00   |  | 0  | 0  | 0  | 0  |
| 01   |  | 1  | 1  | 1  | 0  |
| 11   |  | 0  | 0  | 0  | 0  |
| 10   |  | 0  | 1  | 1  | 1  |

$$f = a'c'd + bc'd + bcd' + acd'$$

 

*Hardware cost*


Number of gates: 5

Total number of inputs: 16

## 2 Factor the expression

$$f = a'c'd + bc'd + bcd' + acd'$$

$$f = c'd(a' + b) + cd'(a + b)$$

 

*Hardware cost*

Number of gates: 5

Total number of inputs: 12




3 Find the minimized POS (product-of-sums) expression; find its cost

| AB \ CD |    | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|----|
| CD      | 00 | 0  | 0  | 0  | 0  |
|         | 01 | 1  | 1  | 1  | 0  |
|         | 11 | 0  | 0  | 0  | 0  |
|         | 10 | 0  | 1  | 1  | 1  |

$$f' = c'd' + ab'c' + cd + a'b'c$$

$$f = (c+d)(a'+b+c)(c'+d')(a+b+c')$$

 

*Hardware cost*

Number of gates: 5


Total number of inputs: 14

#### 4 Factor the expression

$$f = (c+d)(a'+b+c)(c'+d')(a+b+c')$$

$$f = [c + d(a'+b)] [c' + d'(a+b)]$$

$$f = (c + a'd + bd) (c' + ad' + bd')$$

 

*Hardware cost*

Number of gates: 7

Total number of inputs: 16


# All the Results we Got

1

Hardware cost

Number of gates: 5

Total number of inputs: 16

 


2

Hardware cost

Number of gates: 5

Total number of inputs: 12

 


Lowest Hardware Cost

3

Hardware cost

Number of gates: 5

Total number of inputs: 14

 


4

Hardware cost

Number of gates: 7

Total number of inputs: 16

 

# Find the Circuit with the Smallest Cost

- We have the function:  $F(A,B,C,D) = \sum m(1, 3, 5, 9, 15)$

| AB \ CD |    | AB |    |    |    |
|---------|----|----|----|----|----|
|         |    | 00 | 01 | 11 | 10 |
| CD      | 00 | 0  | 0  | 0  | 0  |
|         | 01 | 1  | 1  | 0  | 1  |
|         | 11 | 1  | 0  | 1  | 0  |
|         | 10 | 0  | 0  | 0  | 0  |

$$F = A'C'D + A'BC'D + A'B'D + ABCD$$

# gates: 5

# inputs: 18

Factor:

$$F = C'D(A' + A'B) + D(A'B' + ABC)$$

#gates: 8

#inputs: 18

# Find the Circuit with the Smallest Cost

- We have the function:  $F(A,B,C,D) = \sum m(1, 3, 5, 9, 15)$
- Find the expression of  $f'$  and convert it to POS

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 0  | 0  | 0  | 0  |
| 01      | 1  | 1  | 0  | 1  |
| 11      | 1  | 0  | 1  | 0  |
| 10      | 0  | 0  | 0  | 0  |

$$F' = D' + ABC' + A'BC + AB'C$$

$$F = D (A' + B' + C)(A + B' + C')(A' + B + C')$$

# gates: 4

# inputs: 13

Factor:

$$\begin{aligned} F &= D[B' + (A' + C)(A + C')](A' + B + C') \\ &= D(B' + A'C' + AC)(A' + B + C') \end{aligned}$$

#gates: 5


#inputs: 13

Out of the 4 cases we found,  
this is the smallest cost.

# NAND Gate

- NAND gate is a “Not AND” gate
- Invert of AND

| A | B | AND | NAND |
|---|---|-----|------|
| 0 | 0 | 0   | 1    |
| 0 | 1 | 0   | 1    |
| 1 | 0 | 0   | 1    |
| 1 | 1 | 1   | 0    |

 

NAND gate is an AND gate with an inverter on the output




This is the symbol of the NAND gate  
The bubble (round circle) on the output signifies an inverter

# NOR Gate

- NOR gate is a “Not OR” gate
- Invert of OR

| A | B | OR | NOR |
|---|---|----|-----|
| 0 | 0 | 0  | 1   |
| 0 | 1 | 1  | 0   |
| 1 | 0 | 1  | 0   |
| 1 | 1 | 1  | 0   |

 


NOR gate is an OR gate with an inverter on the output




This is the symbol of the NOR gate  
The bubble (round circle) on the output signifies an inverter
 
## Using NAND gates to make an inverter, an AND gate and a NOR gate



An inverter

 


An AND gate

| A | B | NAND |
|---|---|------|
| 0 | 0 | 1    |
| 0 | 1 | 1    |
| 1 | 0 | 1    |
| 1 | 1 | 0    |

NAND is called a functionally complete set of gates.

 Using NAND, we can implement any logic circuit.



An OR gate


By DeMorgan's


 
# Functionally Complete Set of Gates

- A set of gates is called functionally complete
  - We can implement any logic circuit using gates from this set
- This set {AND, OR, INVERTER} is functionally complete
- This set {NAND} is functionally complete
- This set {NOR} is functionally complete
- This set {AND, INVERTER} is functionally complete


Using AND and NOT, we can make an OR gate:



# NAND-only Circuit & NOR-only Circuit

- NAND-only circuit
  - A circuit that has NAND gates only
- NOR-only circuit
  - A circuit that has NOR gates only
- Any logic function can be implemented using NAND gates only
- Any logic function can be implemented using NOR gates only

# Things to Remember

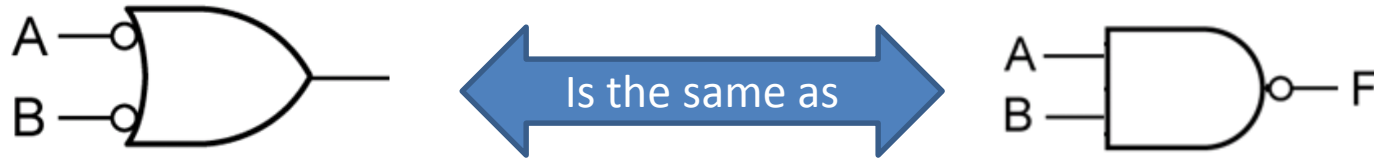

$$A' + B' = [(A' + B')']' = [A.B]'$$


---




$$A'.B' = [(A'.B')']' = [A+B]'$$
 
# Transforming a Circuit to NAND-only Circuit



- Write the sum-of-product form of the function
- Draw the diagram
- Replace all the gates by NAND




Sum-of-products

 

  
These bubbles will  
cancel out; these  
circuits are equivalent



This is equivalent to a  
NAND gate

 

 
$$\begin{aligned} A' + B' &= [(A' + B')']' \\ &= (A \cdot B)' = A \text{ nand } B \end{aligned}$$



 
# Transforming a Circuit to NOR-only Circuit



- Write the product-of-sums form of the function
- Draw the diagram
- Replace all the gates by NOR




Product-of-sums

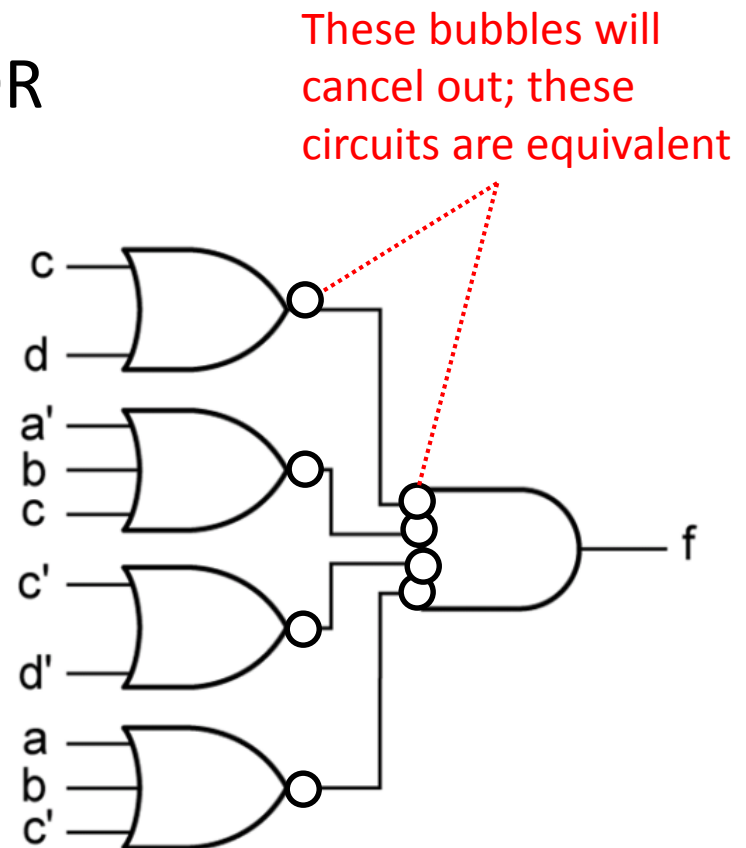

  These bubbles will  
cancel out; these  
circuits are equivalent




This is equivalent to a  
NOR gate

 


$$A'B' = [(A'B')']'$$

$$= (A+B)' = A \text{ nor } B$$

 


 
# Transforming an Multi-Level Circuit to NAND-only Circuit

$$F = a' [b' + c(d+e') + f'g'] + hi'j + k$$




 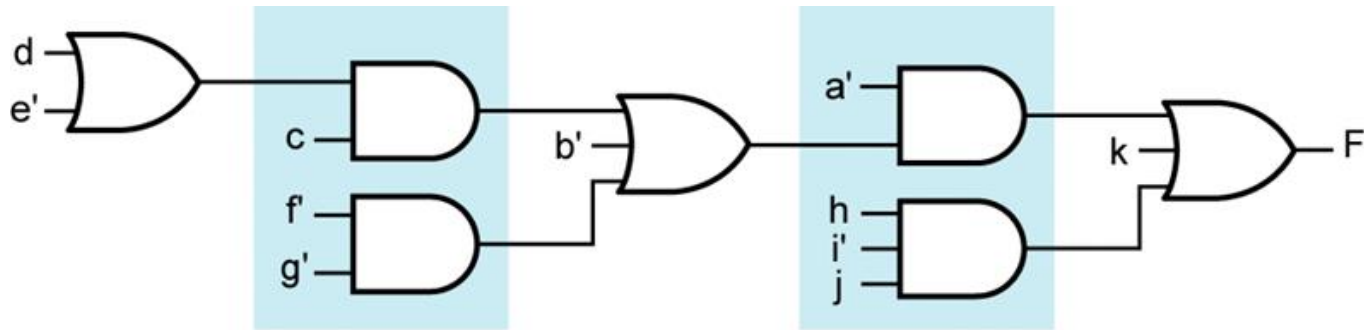We need to transform this circuit to a NAND-only circuit






 Add the bubble (inverters) on the output of AND and input of OR. Complement signals on inputs of OR.




 The AND already became NAND. The OR gates with bubbles on the input are equivalent to NAND




 
# Transforming an Multi-Level Circuit to NOR-only Circuit


$$F = a' \cdot [a(e+g) + b'] \cdot [c+(a' \cdot c')]$$



  
We need to transform this circuit to a NOR-only circuit



 Add the bubble (inverters) on the output of OR and input of AND. Complement signals on inputs of AND.



 The OR already became NOR. The AND gates with bubbles on the input are equivalent to NOR



# Multiple-Output Circuits

- We have these three functions


$$F_1(A, B, C, D) = \Sigma m(11, 12, 13, 14, 15)$$

$$F_2(A, B, C, D) = \Sigma m(3, 7, 11, 12, 13, 15)$$

$$F_3(A, B, C, D) = \Sigma m(3, 7, 12, 13, 14, 15)$$


- We need to draw a circuit to implement them
 
$$F_1(A, B, C, D) = \sum m(11, 12, 13, 14, 15)$$




$F_1$
 
$$F_3(A, B, C, D) = \sum m(3, 7, 12, 13, 14, 15)$$



$F_3$
 
$$F_2(A, B, C, D) = \sum m(3, 7, 11, 12, 13, 15)$$




$F_2$

Number of gates: 9

Total # inputs: 21

Minimize every function separately

 

## Consider common terms

$F_1$


| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    |    | 1  |    |
| 01      |    |    | 1  |    |
| 11      |    |    | 1  | 1  |
| 10      |    |    | 1  |    |

$F_2$

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    |    | 1  |    |
| 01      |    |    | 1  |    |
| 11      | 1  | 1  | 1  | 1  |
| 10      |    |    |    |    |

$F_3$

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    |    | 1  |    |
| 01      |    |    | 1  |    |
| 11      | 1  | 1  | 1  |    |
| 10      |    |    | 1  |    |

 

Number of gates: 7  
Total # inputs: 18

Previously,  
Number of gates: 9  
Total # inputs: 21

# Example 2




- We have these three functions

$$F_1(A, B, C, D) = \Sigma m(2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$

$$F_2(A, B, C, D) = \Sigma m(2, 3, 5, 6, 7, 10, 11, 14, 15)$$

$$F_3(A, B, C, D) = \Sigma m(6, 7, 8, 9, 13, 14, 15)$$

   - We need to draw a circuit to implement them



$$F_1 = AB' + BD + B'C$$




$$F_2 = A'BD + C$$

$$F_3 = AB'C' + ABD + BC$$

Number of gates: 10

total number of inputs: 25



   

$$F_1 = AB'C' + A'BD + ABD + A'B'C + AB'C$$




$$F_2 = A'BD + A'B'C + BC + AB'C$$

$$F_3 = AB'C' + ABD + BC$$

Number of gates: 9

total number of inputs: 29

It turns out there is a better solution.

   


#gates: 8, total # inputs: 22.

Taking common terms does not guarantee obtaining the least cost implementation, but sometimes it helps.

In this class, we do not cover the method to obtain the minimum hardware cost for the multiple-output function. Trial-and-error can be made to find a function with lesser hardware cost.
 
# Convert Multiple-Output Function to NOR-only Circuit



Start by putting bubbles at the output of OR gates.

Put a bubble at the input of the AND gates. Complement the signals at the input of AND gates.

The AND gate with bubbles on the input can be replaced with a NOR gate.

